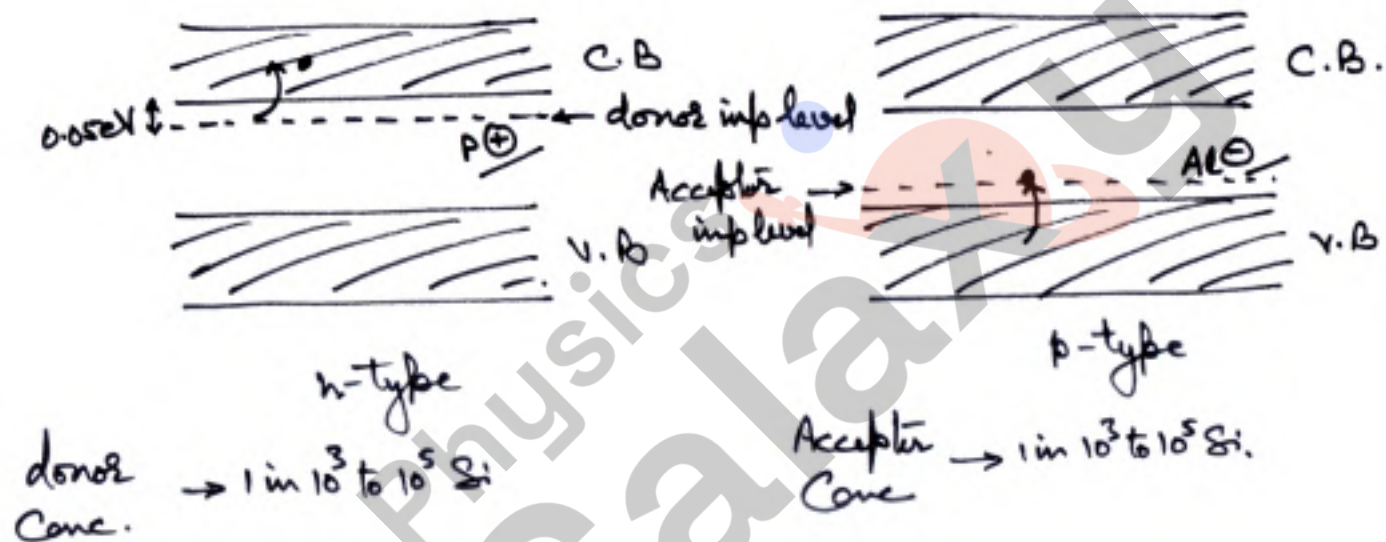


**Revision Booster
WORKSHOP
for
NEET & JEE Main**


Semiconductors

Notes of Revision Booster Workshop for JEE Main & NEET
9000+ Classes available on PHYSICS GALAXY Mobile app


QUESTIONS BASED ON
BAND GAPS IN p-TYPE AND n-TYPE SEMICONDUCTORS



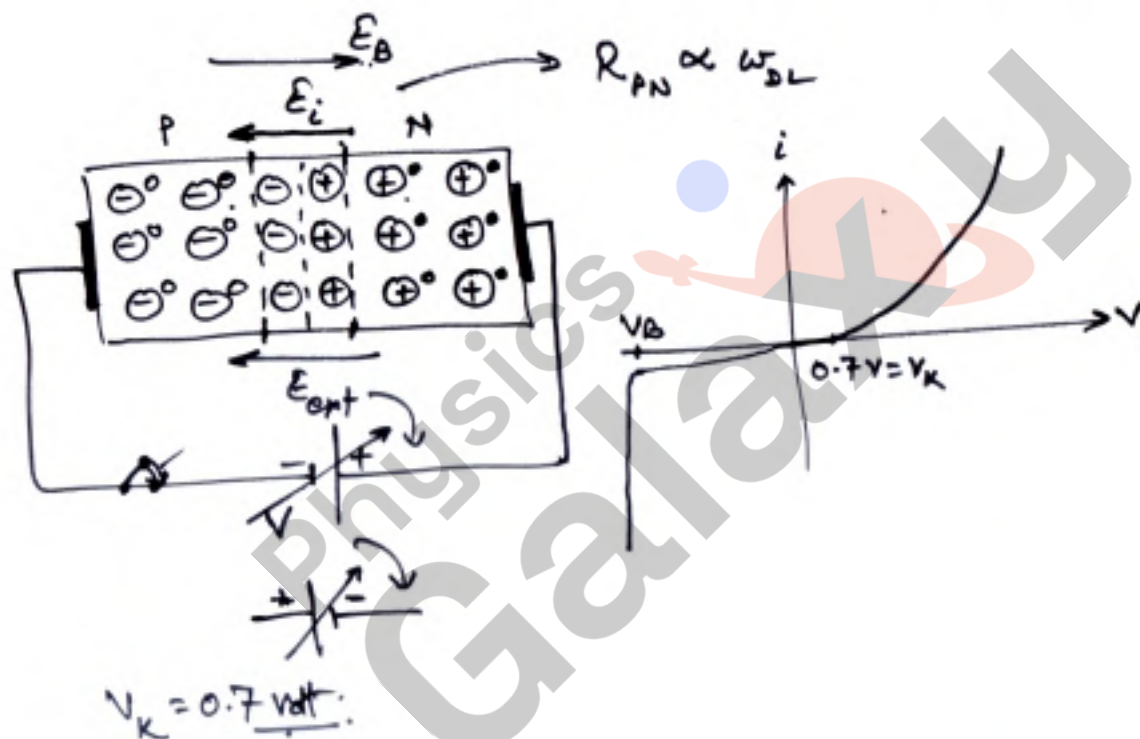QUESTIONS BASED ON
ELECTRIC FIELD IN DEPLETION LAYER OF A p-n JUNCTION



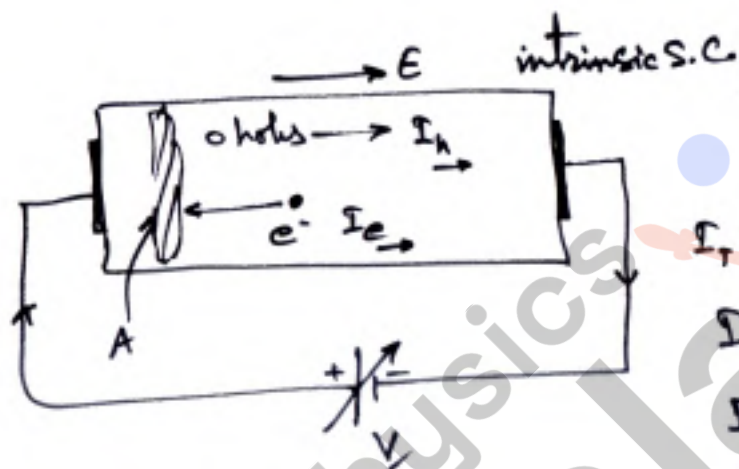QUESTIONS BASED ON
CONDUCTION IN SEMICONDUCTOR



$$\underline{V_d = \mu E.}$$

$$I_T = I_e + I_h$$


$$I = A [J_e + J_h] -$$

$$I = An_i e (v_{de} + v_{dh}) -$$

$$I = An_i e E (\mu_e + \mu_h) -$$


$$I = AE (\sigma_e + \sigma_h) -$$

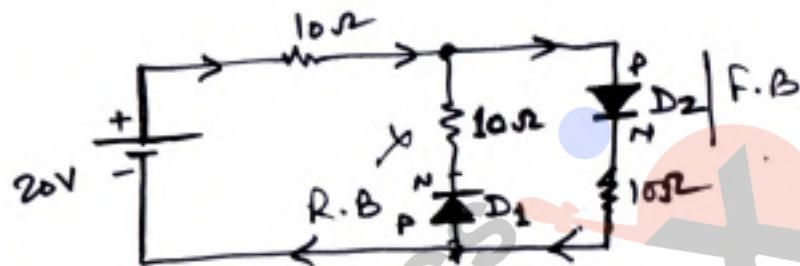QUESTIONS BASED ON
IDEAL DIODES IN CIRCUITS




$$I = \frac{20}{10+10} = 1 \text{ A.}$$

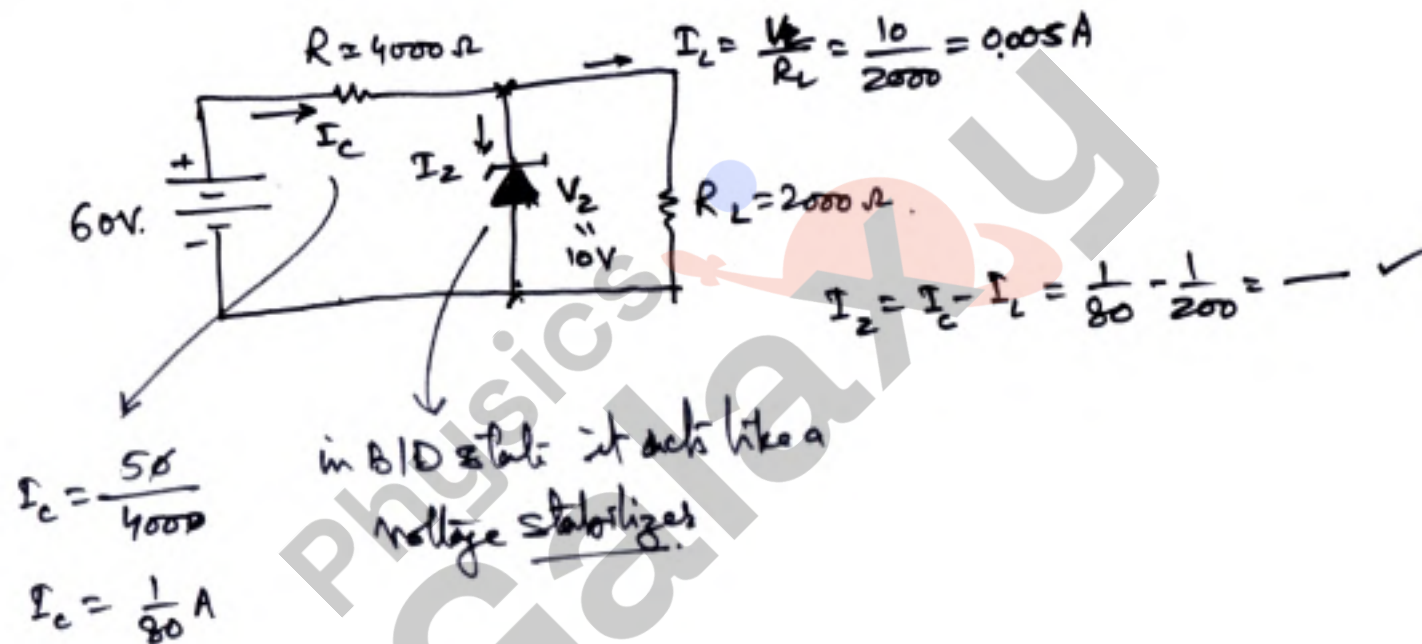QUESTIONS BASED ON
CIRCUITS WITH ZENER DIODE




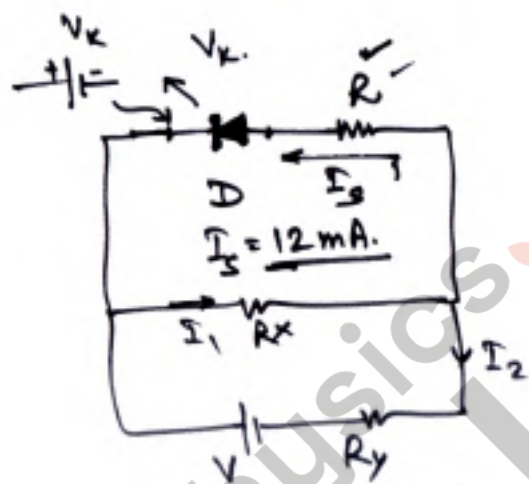QUESTIONS BASED ON
SAFE CURRENT LIMIT OF A DIODE



For safe limit of a diode
Series resistance
is used

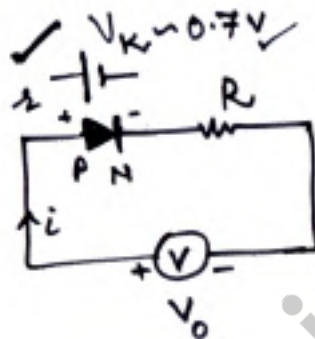QUESTIONS BASED ON
FORWARD BIASED REAL DIODE IN CIRCUIT



Ckt current

$$i = \frac{V_0 - V_K}{R} \quad (\text{if there is no resistance in diode})$$

otherwise

$$i = \frac{V_0 - V_K}{R + r_0}$$

QUESTIONS BASED ON
ZENER DIODES IN SERIES

