

**Revision Booster  
WORKSHOP  
for  
NEET & JEE Main**


---

**Current &  
Capacitance**

---

Notes of Revision Booster Workshop for JEE Main & NEET  
**9000+ Classes available on PHYSICS GALAXY Mobile app**

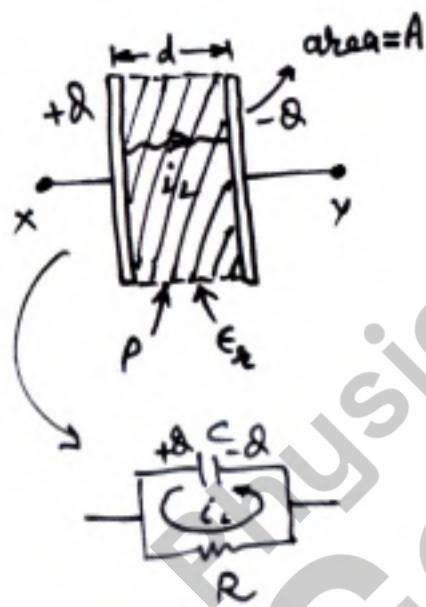QUESTIONS BASED ON  
**# DISCHARGE IN A LEAKY CAPACITOR**



$$R_{xy} = \frac{\rho d}{A}$$


$$C_{xy} = \frac{\epsilon_0 \epsilon_r A}{d}$$

← Parallel


$$i_L = \frac{Q}{RC} e^{-t/RC}$$

time constant  $\tau = RC = \underline{\underline{\rho \epsilon_0 \epsilon_r}}$

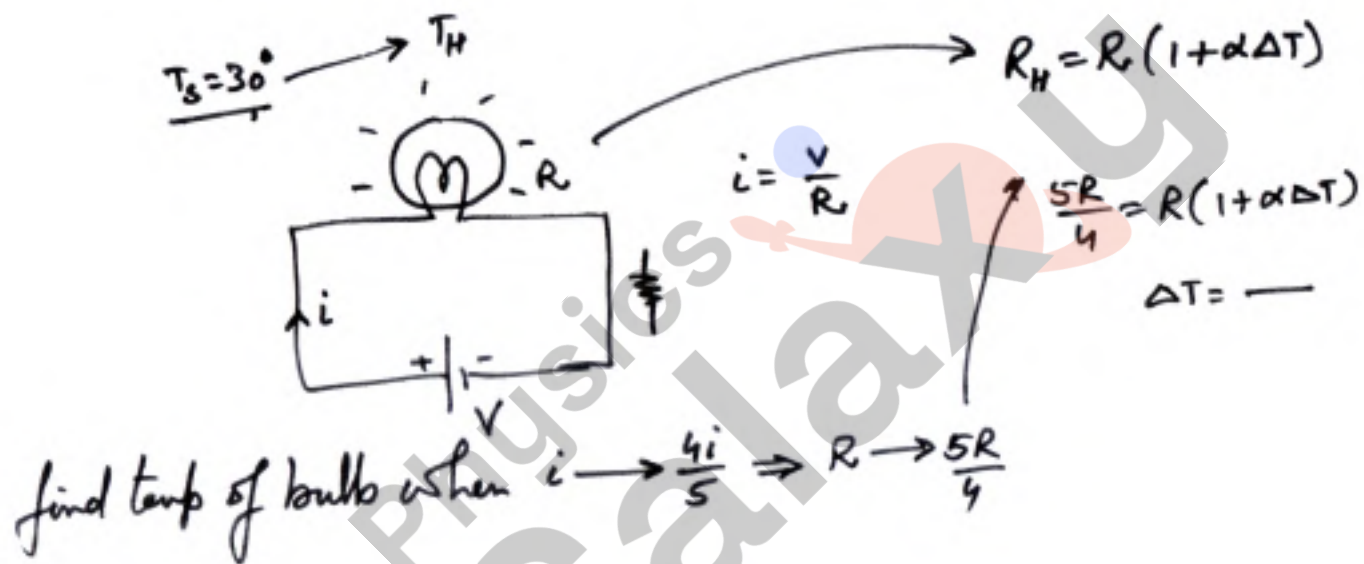QUESTIONS BASED ON  
**# VARYING RESISTANCE OF A BULT**



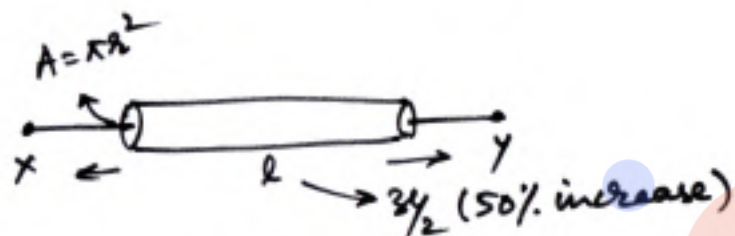QUESTIONS BASED ON  
**# VARIATION IN RESISTANCE BY DEFORMATION**



$V \rightarrow \text{const}$   
 $V = lA$   
 $\frac{3l}{2} \cdot \frac{2A}{3}$


$$R_{xy} = \frac{\rho l}{A}$$

new resistance  $R_{\text{new}} = \frac{\rho(\frac{3l}{2})}{\frac{2A}{3}} = \frac{9}{4} R_{xy} = 2.25 R_{xy}$   
 125% increase in resistance.




If temp is inc by  $\Delta T$   
 if  $\rho \rightarrow \text{constant}$

$$R_{\text{new}} = \frac{\rho l(1 + \alpha \Delta T)}{A(1 + 2\alpha \Delta T)} = \frac{R(1 + \alpha \Delta T)}{1 + 2\alpha \Delta T}$$

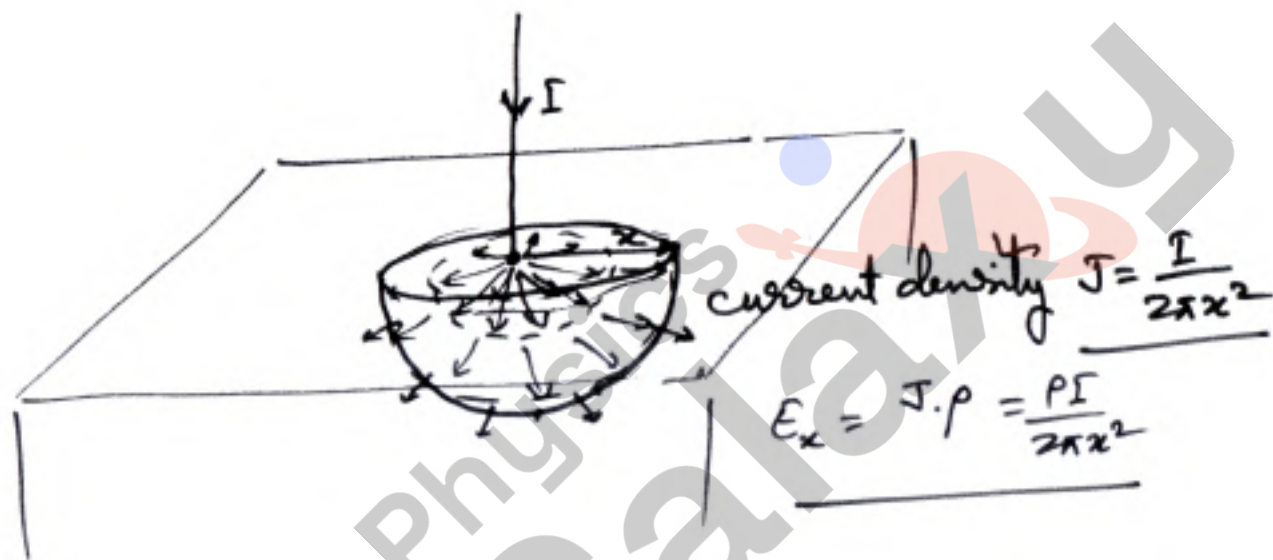QUESTIONS BASED ON  
**# ELECTRIC CURRENT SPREADING IN VOLUME**



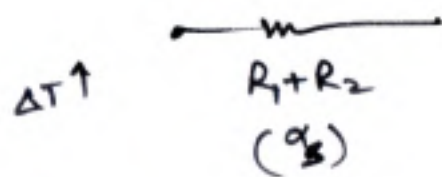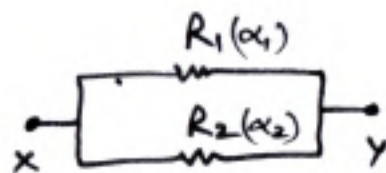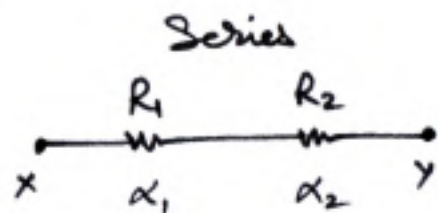QUESTIONS BASED ON  
**# EQUIVALENT TEMPERATURE COEFFICIENT OF RESISTANCE**



$$(R_1 + R_2) = R_1(1 + \alpha_1 \Delta T) + R_2(1 + \alpha_2 \Delta T)$$

$$(R_1 + R_2)(1 + \alpha_s \Delta T) = R_1 + R_2 + R_1 \alpha_1 \Delta T + R_2 \alpha_2 \Delta T$$

$$\alpha_s = \frac{R_1 \alpha_1 + R_2 \alpha_2}{R_1 + R_2}$$


An equivalent circuit diagram showing a single resistor with resistance  $\frac{R_1 R_2}{R_1 + R_2}$  and temperature coefficient  $(\alpha_p)$ .

$$\frac{1}{R_{eq}} = \frac{1}{R_1(1 + \alpha_1 \Delta T)} + \frac{1}{R_2(1 + \alpha_2 \Delta T)}$$

$$\left( \frac{R_1 R_2}{R_1 + R_2} \right) (1 + \alpha_p \Delta T) = \frac{R_1 R_2}{R_1 + R_2}$$

$$\alpha_p = \frac{R_1 \alpha_1 + R_2 \alpha_2}{R_1 + R_2}$$

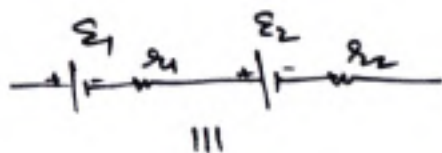
QUESTIONS BASED ON  
**# CIRCUIT SOLVING USING CALL COMBINATIONS**





III

$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2$

$r_1 + r_2 = r_{eq}$

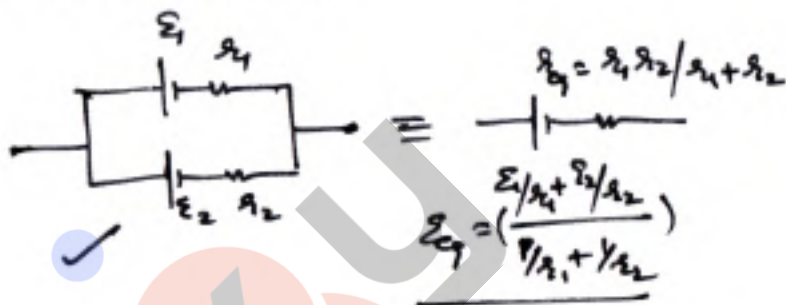

Sol:  $\Sigma_{4\Omega} = 9$

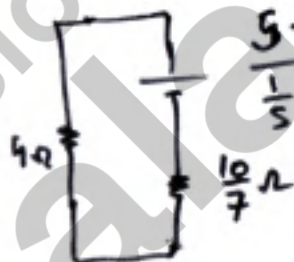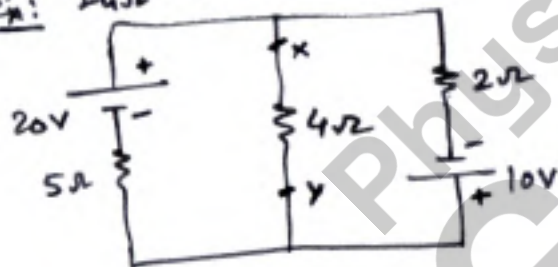


$\frac{5-4}{\frac{1}{5} + \frac{1}{2}} = \mathcal{E}_{eq} = \frac{10}{7} \text{ V}$

$I = \frac{10/7}{4 + 10/7} \text{ A}$  dir

QUESTIONS BASED ON  
**# FUSING OF A BULB IN CIRCUIT**

$$\begin{array}{c} \downarrow \\ 200\text{V}, 100\text{W} \\ V_B \quad P_B \end{array} \longrightarrow R_B = \frac{V^2}{P}$$

Sol:

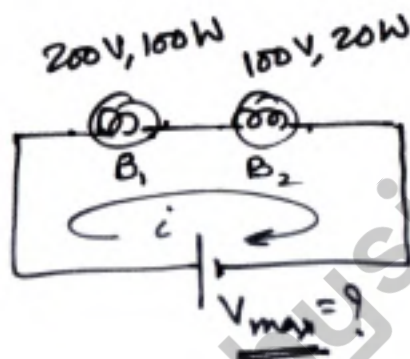

$$R_1 = \frac{(200)^2}{100} = 400 \Omega$$

$$R_2 = \frac{(100)^2}{20} = 500 \Omega$$



$$i = \frac{V_m}{900}$$

$$V_1 = \frac{V_m}{900} \times 400 \leq 200 \longrightarrow V_m = \dots$$

$$V_2 = \frac{V_m}{900} \times 500 \leq 100 \longrightarrow V_m = \dots$$

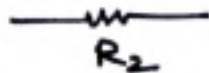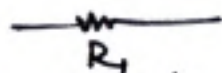QUESTIONS BASED ON  
**# HEATING COILS COMBINATION**

$t_1 \rightarrow$  water Boil  $\leftarrow t_2$




$$i^2 R_1 t_1 = H = i^2 R_2 t_2 \quad \text{--- (1)}$$

$$\frac{V^2}{R_1} t_1 = \frac{V^2}{R_2} t_2 = H$$

Case I  $\rightarrow$   $i$  Const

Case II  $\rightarrow$   $V$  Const

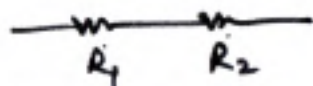

$$\left( \frac{V^2}{R_1 + R_2} \right) t = H$$

$$i^2 (R_1 + R_2) t = H$$

$$\left( \frac{\frac{V^2 t_1}{H} + \frac{V^2 t_2}{H}}{\frac{V^2}{H}} \right) = \frac{H}{t}$$


$$\frac{H}{t_1} + \frac{H}{t_2} = \frac{H}{t}$$

$$\frac{H}{t_1 + t_2} = \frac{H}{t}$$

$$\underline{t_s = \frac{t_1 t_2}{t_1 + t_2}}$$

$$\underline{t = t_1 + t_2}$$

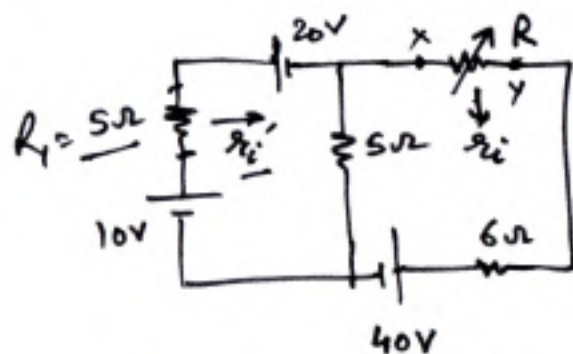QUESTIONS BASED ON  
**# MAXIMUM POWER IN A CIRCUIT**



for max power in a "variable resistance"

$$R_v = r_i$$

$$R_v = 6 + 2.5 = 8.5 \Omega$$

if Power in  $R$ , is to be maximised.  
 then  $r_i$  is to be minimised.

$$r_i = \frac{5(6+R)}{5+(6+R)}$$


$$\left(\frac{1}{r_i}\right) = \frac{1}{5} + \frac{1}{6+R} \rightarrow [0] \text{ Ans}$$

QUESTIONS BASED ON  
**# CURRENT DENSITY IN SPHERICAL OR CYLINDRICAL CONDUCTORS**

$dR = \frac{\rho dx}{4\pi x^2}$   
 $R = \int dR = \frac{\rho}{4\pi} \int_a^b \frac{dx}{x^2}$   
 $R = \frac{\rho}{4\pi} \left[ \frac{1}{a} - \frac{1}{b} \right]$   
 $I = \frac{V_x - V_y}{R}$   
 $J_x = \frac{I}{4\pi x^2} \text{ A/m}^2$   
 $E_x = \rho J_x$

$dR = \frac{\rho \cdot dx}{2\pi x L}$  ✓  
 $J_x = \frac{I}{2\pi x L}$   
 $I = \frac{V_x - V_y}{R}$  ✓

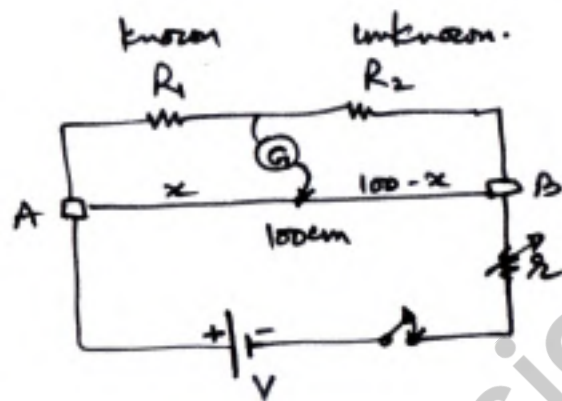QUESTIONS BASED ON  
# METER BRIDGE FOR UNKNOWN RESISTANCES





for null pt  $\frac{R_1}{x} = \frac{R_2}{100-x}$

$x = \frac{R_1}{R_2} \times 100$

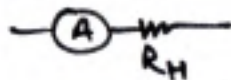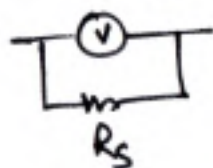QUESTIONS BASED ON  
**# AMMETER REPLACING A VOLTMETER**

$\downarrow$   
 $R \rightarrow \text{low}$


$\downarrow$   
 $R \rightarrow \text{High}$




$$R_V = R_A + R_H$$

$$R_A = \frac{R_S R_V}{R_S + R_V}$$

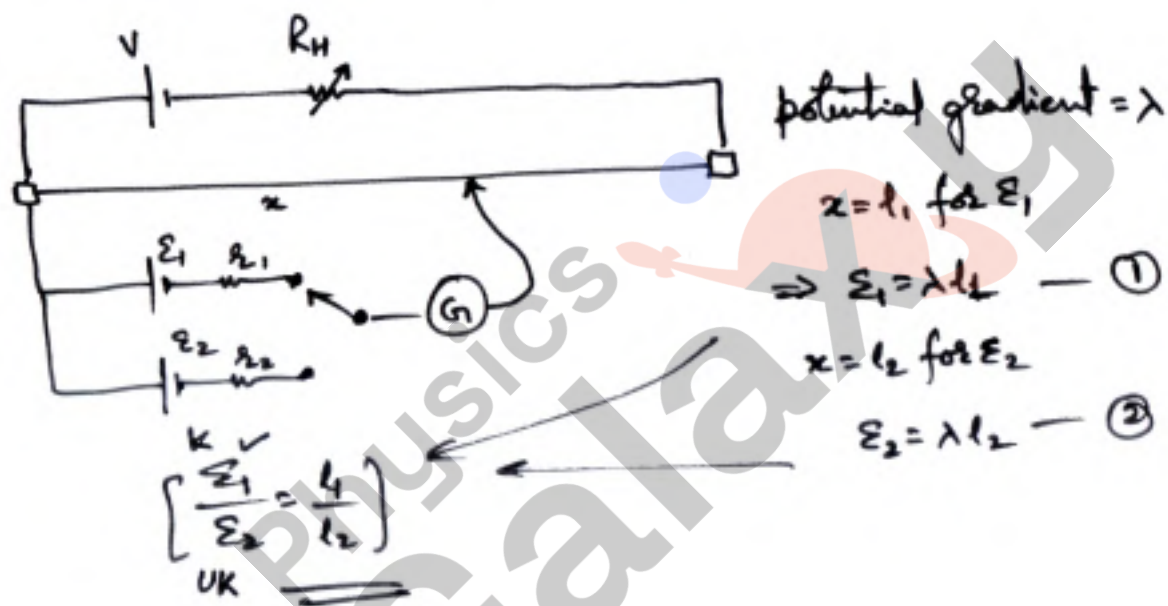QUESTIONS BASED ON  
**# CELL COMPARISON IN A POTENTIOMETER**



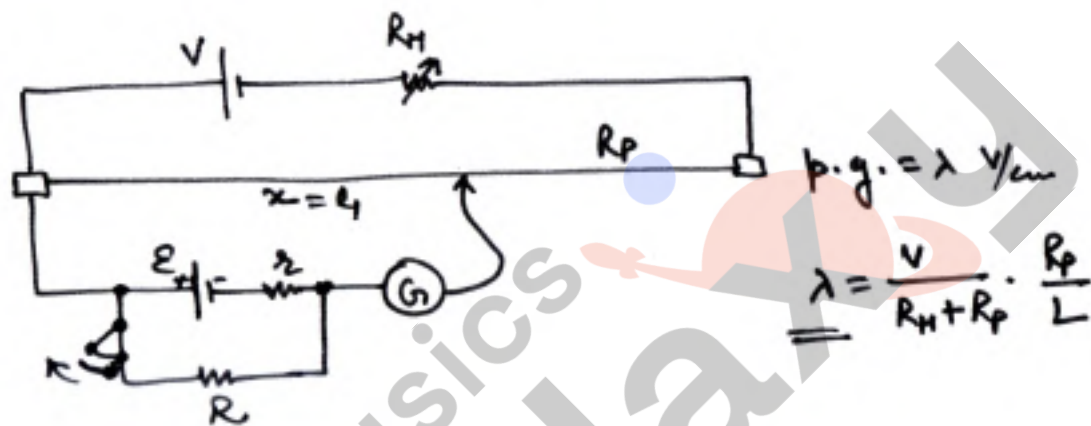QUESTIONS BASED ON  
# INTERNAL RESISTANCE BY A POTENTIOMETER




at  $x = l_1$ ,  $\underline{E = \lambda l_1}$  — (1)

after  $R$  is connected

at  $x = l_2$ ,  $\underline{E - ir = \lambda l_2}$

$$\frac{ER}{r+R} = \lambda l_2 \text{ — (2)}$$

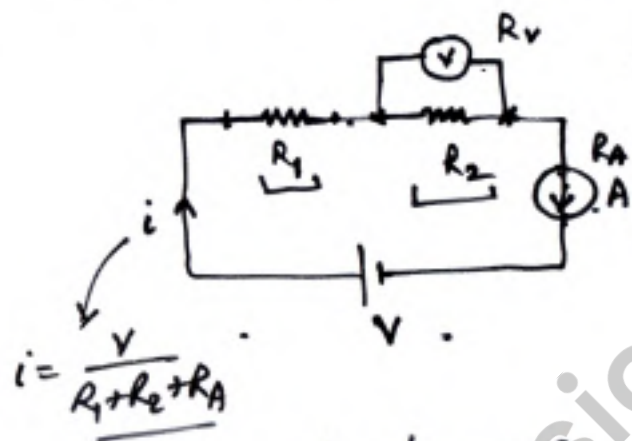QUESTIONS BASED ON  
**# ERROR IN VOLTMETER OR AMMETER**



Error in reading of  $V = ?$

$$V_{\text{Reading}} = i \left( \frac{R_v R_2}{R_v + R_2} \right)$$


$$= \left( \frac{V}{R_1 + \frac{R_v R_2}{R_v + R_2}} \right) \left( \frac{R_v R_2}{R_v + R_2} \right)$$

In absence of  
 voltmeter

$$V_{\text{actual}} = \frac{V}{R_1 + R_2} \cdot R_2$$

$$\% \text{ error} = \frac{|V_a - V_r|}{V_a} \times 100\%$$

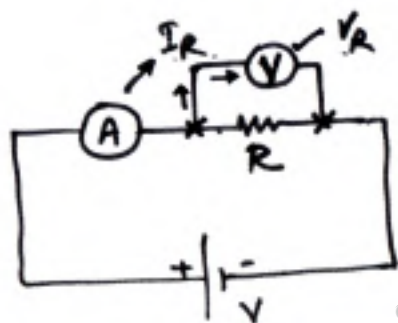QUESTIONS BASED ON  
# EFFECT ON MEASURED VALUE OF R DUE TO V AND A




meas value of Resistance

$$\rightarrow R_m = \frac{V_R}{I_R}$$

here  $I_R > I_{\text{actual } R} \Rightarrow R_{\text{meas}} < R_{\text{actual}}$

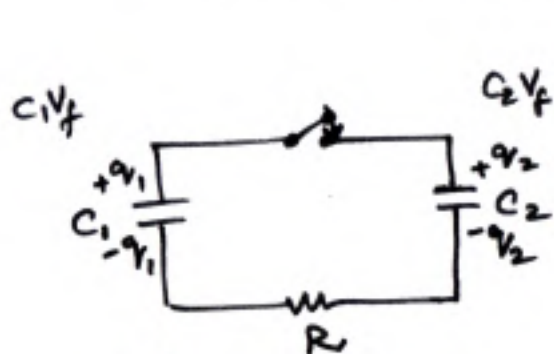QUESTIONS BASED ON  
**# HEAT PRODUCED IN CLOSING THE SWITCH**



$$\left[ V_f = \frac{q_1 + q_2}{C_1 + C_2} \right]$$

$$U_i = \frac{q_1^2}{2C_1} + \frac{q_2^2}{2C_2}$$


$$U_f = \frac{1}{2} (C_1 + C_2) V_f^2$$

$$H = U_i - U_f$$

alternative

$$H = \frac{\Delta q_1^2}{2C_1} + \frac{\Delta q_2^2}{2C_2}$$

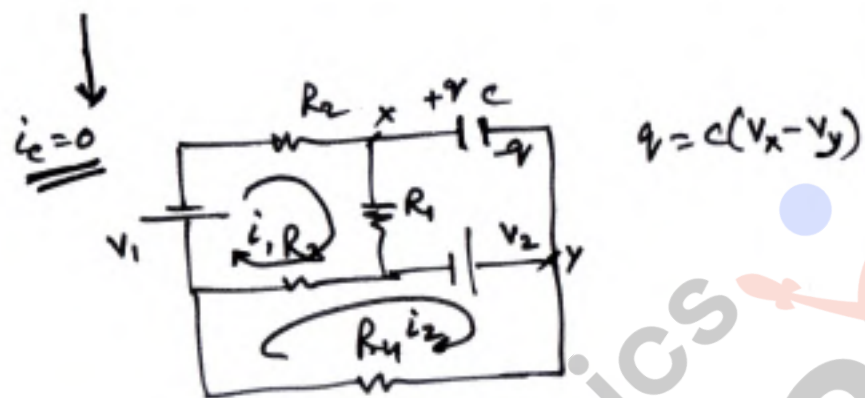
QUESTIONS BASED ON  
**# STEADY STATE OF CAPACITOR IN ELECTRIC CIRCUIT**




in SS  $C \rightarrow$

Physics  
**Galaxy**

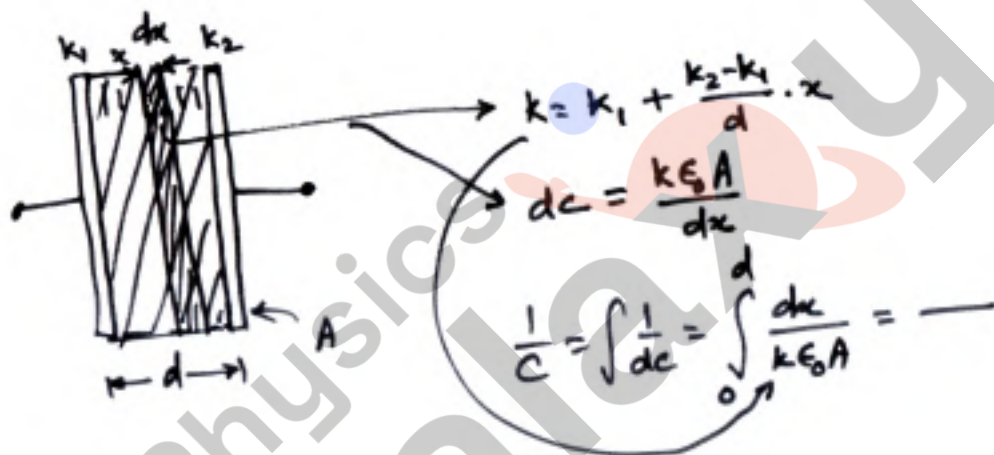QUESTIONS BASED ON  
# DIELECTRIC VARIATION IN CAPACITORS



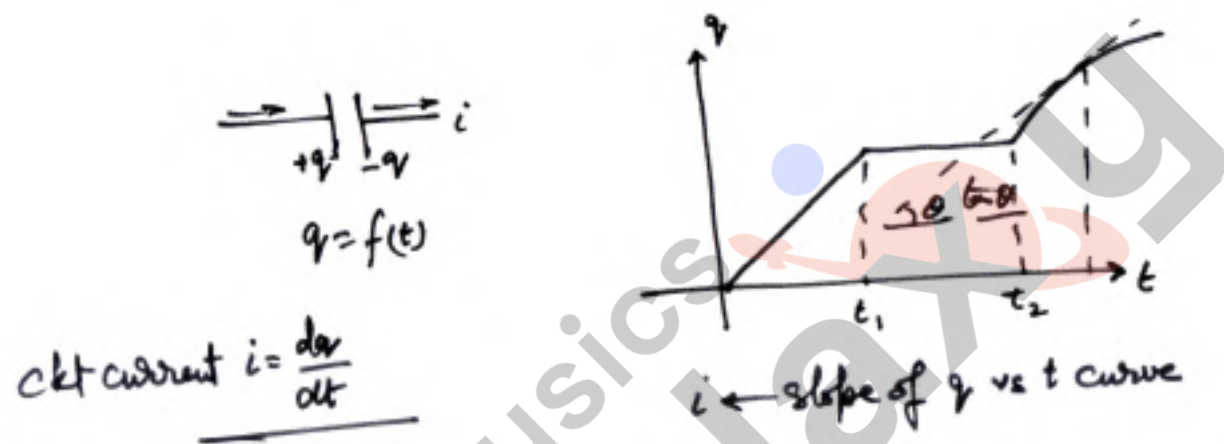QUESTIONS BASED ON  
**# CHARGE VARIATION ON PLATES OF A CAPACITOR**




QUESTIONS BASED ON  
**# VOLTAGE RATING OF A CAPACITOR**

$V_{max}$  ← causes dielectric breakdown.



$V_{m1}$

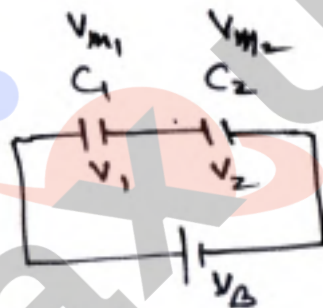

∴ find  $V_B$  max for which  
 both the capacitors will withstand


$$V_{m1} = V_1 = \frac{C_2 V_B}{C_1 + C_2} \quad ; \quad V_2 = \frac{C_1 V_B}{C_1 + C_2} = V_{m2}$$

$$V_B = \underline{\quad}$$

$$V_B = \underline{\quad}$$


whichever is less is the max permissible  
 value of  $V_B$ .

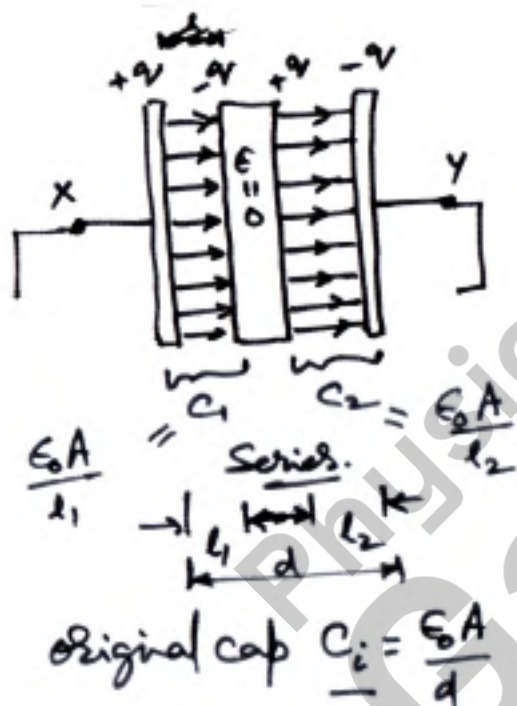QUESTIONS BASED ON  
**# METAL PLATE INSERTED IN A CAPACITOR**




$$C_{xy} = \frac{q_1}{q_1 + q_2}$$

QUESTIONS BASED ON  
# CAPACITANCE GRID

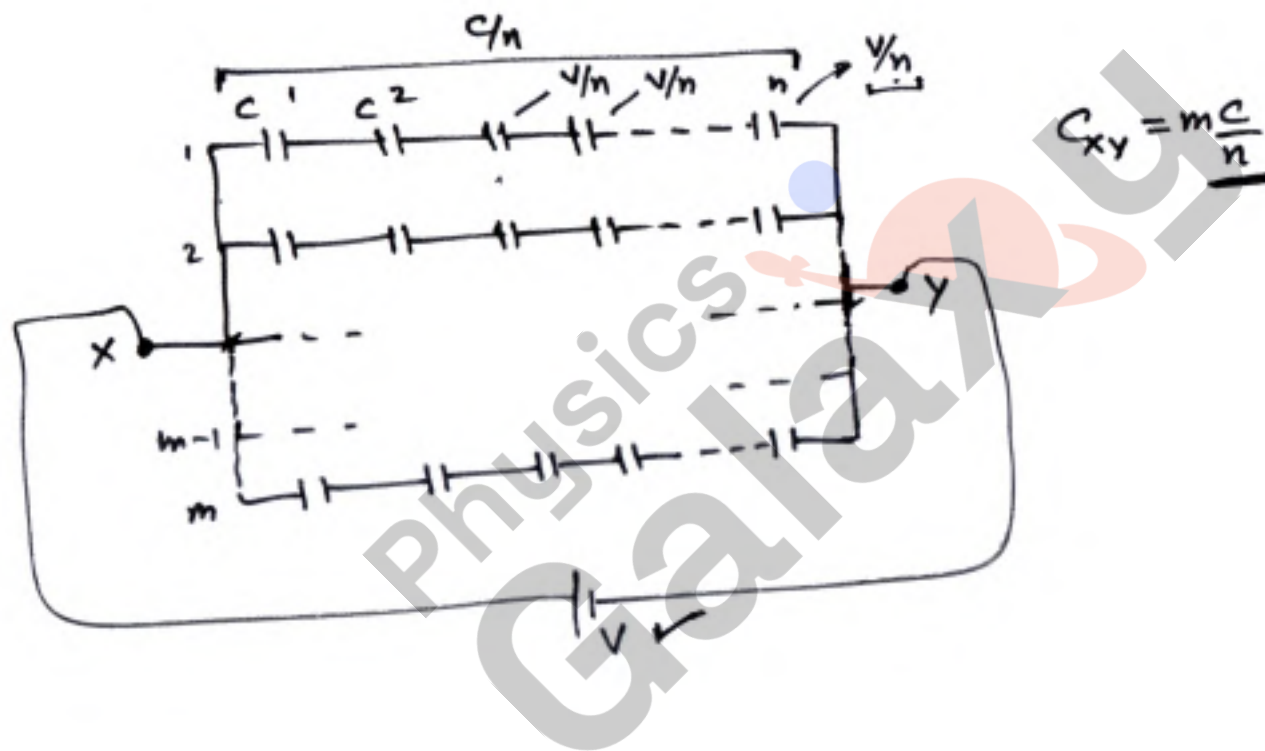

QUESTIONS BASED ON  
# BATTERY GRID

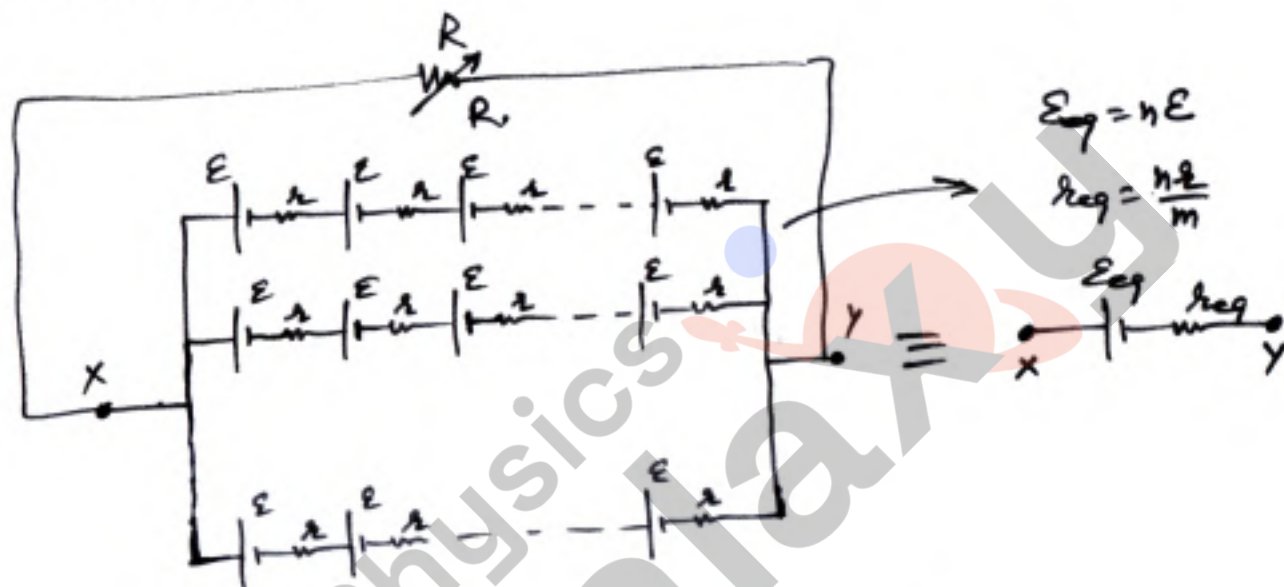

$$E_{eq} = nE$$

$$r_{eq} = \frac{nr}{m}$$

for max power in  $R$ , we use  $R = \frac{nr}{m}$ .

QUESTIONS BASED ON  
# WORK DONE BY BATTERY IN CHARGING A CAPACITIVE CIRCUIT

